

# Applications of Linear Differential Equations with Constant Coeff's. (LDWCC) (1)

## Electrical circuit

The formation of Differential Equation for an electric circuit depends upon the following laws.

(i)  $i = \frac{dq}{dt}$

(ii) Voltage drop across resistance ( $R$ ) =  $Ri$

(iii) Voltage drop across inductance ( $L$ ) =  $L \frac{di}{dt}$

(iv) Voltage drop across Capacitance ( $C$ ) =  $\frac{q}{C}$


## Kirchoff's Law

Voltage Law : The algebraic sum of the voltage drop around any closed circuit is equal to the resultant electromotive force in the circuit.

(2)


Current Law : At a junction (or) nodes,  
Current Coming is equal to Current going.

L-R Series circuit

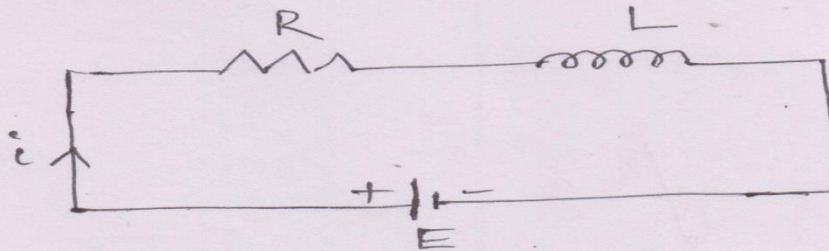

by voltage Law,  $Ri + L \frac{di}{dt} = E$

L-R-C circuit

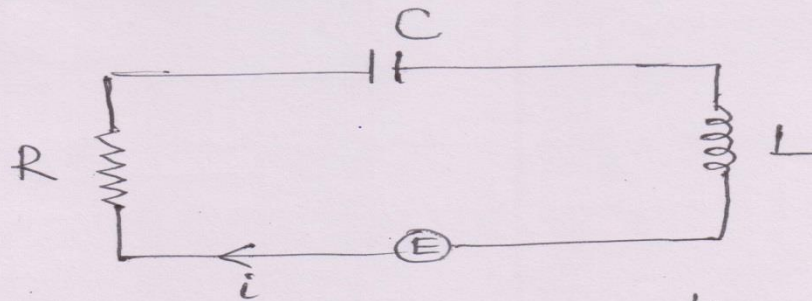

by voltage Law,  $Ri + L \frac{di}{dt} + \frac{q}{C} = E$

(or)  $L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = E$  ( $\because i = \frac{dq}{dt}$ )



① An electric circuit consists of an inductance 0.1 henry, a resistance of 20 ohms and a Condenser of capacitance 25 micro-farads. Find the charge  $q$  and the current  $i$  at any time 't', given that at  $t=0$ ,  $q=0.05$  coulomb,  $i=0$  when  $t=0$

③

Sol: Given  $L = 0.1 \text{ h}$ ,  $R = 20 \Omega$ ,  
 $C = 25 \text{ m.f} = 25 \times 10^{-6} \text{ farad}$

The D.E. for the given data is

$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = 0 \quad \text{--- ①}$$

It's operator form is  $\left[ D^2 + \left( \frac{R}{L} \right) D + \frac{1}{LC} \right] q = 0$  --- ②

$$\text{or } \left[ D^2 + \left( \frac{20}{0.1} \right) D + \frac{1}{(0.1)(25 \times 10^{-6})} \right] q = 0$$

$$\text{Clearly } q_c = e^{-100t} [C_1 \cos(100\sqrt{39}t) + C_2 \sin(100\sqrt{39}t)]$$

$$\therefore q = q_c = e^{-100t} [C_1 \cos(100\sqrt{39}t) + C_2 \sin(100\sqrt{39}t)]$$

When  $t=0$ ;  $q=0.05$  &  $i=0$ , then  $C_1 = 0.05$   
 $C_2 = 0.008$

$$\therefore q = e^{-100t} [0.05 \cos(624.5t) + 0.08 \sin(624.5t)]$$

② An inductor of 2 henries, resistor of 16 ohms and capacitor of 0.02 farads are connected in series with a battery of electromotive force  $E = 100 \sin 3t$ . At  $t=0$ , the charge on the capacitor and current in the circuit are zero. Find the charge and current.

Sol: Given  $L = 2 \text{ h}$ ;  $R = 16 \Omega$ ;  $C = 0.02 \text{ farad}$   
 $E = 100 \sin 3t$ .

The D.E. for the given data is

$$L \frac{d^2 V}{dt^2} + R \frac{dV}{dt} + \frac{V}{C} = E$$

(or) It's operator form is  $\left[ D^2 + \frac{R}{L} D + \frac{1}{LC} \right] V = \frac{E}{L}$  ①

$$(or) \left[ D^2 + \left( \frac{16}{2} \right) D + \left( \frac{1}{2 \times 0.02} \right) \right] V = \frac{100 \sin 3t}{2}$$

Clearly  $V_c = e^{-4t} [C_1 \cos 3t + C_2 \sin 3t]$

$$V_p = \frac{25}{52} [2 \sin 3t - 3 \cos 3t]$$

$$\therefore V = V_c + V_p = e^{-4t} [C_1 \cos 3t + C_2 \sin 3t] + \frac{25}{52} [2 \sin 3t - 3 \cos 3t]$$



(5)

$$\begin{aligned} i = \frac{dq}{dt} &= -4e^{-4t}(C_1 \cos 3t + C_2 \sin 3t) \\ &\quad - 3e^{-4t}(C_1 \sin 3t - C_2 \cos 3t) \\ &\quad + \frac{25}{52}(6 \cos 3t + 9 \sin 3t) \end{aligned}$$

when  $t=0$ ,  $q=0$  &  $i=0$

$$\therefore C_1 = 75/52 \quad ; \quad C_2 = 50/52$$

$$\begin{aligned} \therefore q &= \frac{25}{52} e^{-4t} [3 \cos 3t + 2 \sin 3t] \\ &\quad + \frac{25}{52} [2 \sin 3t - 3 \cos 3t] \end{aligned}$$

$$\begin{aligned} i &= \frac{75}{52} [2 \cos 3t + 3 \sin 3t] \\ &\quad - \frac{25}{52} e^{-4t} [17 \sin 3t + 6 \cos 3t] \end{aligned}$$

## Exercise :-

(6)

- ① For an electric circuit with  $L = 0.05$  henry,  $R = 20$  ohms and  $C = 100 \times 10^{-6}$  farad, the applied e.m.f is 100 volts. prove that the charge  $q$  at time ' $t$ ' is given by

$$q(t) = 0.01 - e^{-200t} [0.01 \cos(400t) + 0.02 \sin(400t)]$$

if initially  $q=0$  and  $i=0$

- ② An alternating E.M.F  $E \sin pt$  is applied to a circuit at  $t=0$ . Given the equation for the current  $i$  as  $L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = pE \cos pt$ . Find the current  $i$  when  $CR^2 > 4L$ .